

CPSC 218, 03S Term 2 — Midterm Exam — Solution

1. (10 marks) Circle all of the **zero or more** correct answers for each of the following questions.

1a. How many unique 4-variable Boolean functions are there?

- (a) 4 (b) 16 (c) 64 (d) 256 (e) 65536

(e): 4-variable truth table has 2^4 rows. Viewing the output function-value column as a 2^4 digit binary number, there are 2^{2^4} unique values for this column and thus $2^{2^4} = 2^{16} = 65536$ unique truth tables.

1b. Which of the following are minimal, functionally complete sets of Boolean operators? (Minimal means that no subset is complete.)

- (a) {NAND} (b) {XOR} (c) {AND,NOT,OR} (d) {AND,OR}


(a): NAND is AND+NOT, which is complete. Neither XOR nor AND+OR are complete and AND+NOT+OR is not minimal.

1c. Which operations require different hardware implementations for unsigned and signed-twos-complement numbers?

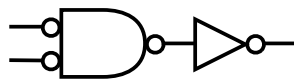- (a) add, ignoring overflow (b) add, testing for overflow (c) shift right
(d) inequality compare (e) load from memory

(b), (c), (d) and (e): Add, ignoring overflow, is the same for both. For the rest: unsigned overflow detected by $C_{out} = 1$, signed overflow detected by sign flip when both operands have same sign; unsigned shift right should set high-order-bit to 0, signed shift right should set high-order-bit to value of high-order-bit before shift; unsigned inequality compare uses magnitude, signed compare ensure that negative numbers are smaller than positive number and otherwise uses magnitude; unsigned load of byte (8 bits) or short (16 bits) requires that high-order bits be *zero extended*, signed load requires that high-order bits be *sign extended*.

1d. What Boolean operator(s) are equivalent to this logic diagram?



- (a) AND (b) OR (c) NAND (d) NOR

(d): Move AND-gate-input circles to the left, changing AND to OR and leaving two circles on OR's output. Move one of the OR-output circles to right canceling INVERTER's circle, changing it into a BUFFER. You're left with a NOR plus a BUFFER which has the same truth table as a NOR.

1e. What boolean functions are equivalent to $f = ab + ab'$?

- (a) a (b) b (c) $a + b$ (d) $(a'b' + a'b)'$ (e) $((a' + b')(a' + b))'$

(a), (d), (e): Using distributive, complement and identity axioms, $ab + ab' = a(b + b') = a(1) = a$. Starting from $ab + ab' = a$ and using identity, complement, distributive, complement and DeMorgan's axioms, $a = a + 0 = a + bb' = (a + b)(a + b') = ((a + b)(a + b'))'' = (a'b' + a'b)'$. Finally, using complement and DeMorgan's axiom, $ab + ab' = (ab + ab')'' = ((a' + b')(a' + b))'$.

2. (6 marks) Consider the following k-map.

		yz			
		00	01	11	10
wx	00	1	0	0	1
	01	1	x	0	1
	11	x	1	x	0
	10	1	1	0	x

		yz			
		00	01	11	10
wx	00	1	0	0	1
	01	1	x	0	1
	11	x	1	x	0
	10	1	1	0	x

2a. Give the simplest boolean function derived directly from this k-map, in sum-of-products form.

$$f = w'z' + wy'$$

2b. Give the simplest boolean function derived directly from this k-map, in product-of-sums form.

$$f = (w'z + wy)' = (w + z')(w' + y')$$

3. (5 marks) What is the main advantage and disadvantage of DRAM compared to SRAM?

3a. Advantage of DRAM:

Small and thus cheap to build. One transistor per bit.

3b. Disadvantage of DRAM:

Slow compared to static RAM due primarily to the fact that reading a bit requires that its entire row first be *pre-charged*.

4. (9 marks) Consider **six-bit**, signed numbers whose values range from -32 to 31.

4a. Use hexadecimal notation to give the representation of -17 in each of the following encodings.

i. sign magnitude:

0x31

ii. two's complement:

0x2f

iii. biased:

0x0f

4b. What is the hexadecimal value of the six-bit, two's complement representation of -17 after it has been shifted to the right twice?

0x3b

4c. Which of the following six-bit (unsigned or two's complement signed) operations result in overflow? Justify your answer.

i. unsigned 0x2a + 0x16?

overflow; carry out of 1

ii. signed 0x2a + 0x16?

no overflow; negative and positive number


iii. signed $0x2a + 0x26$?

overflow; sign change

iv. signed $0x2a + 0x36$?

no overflow

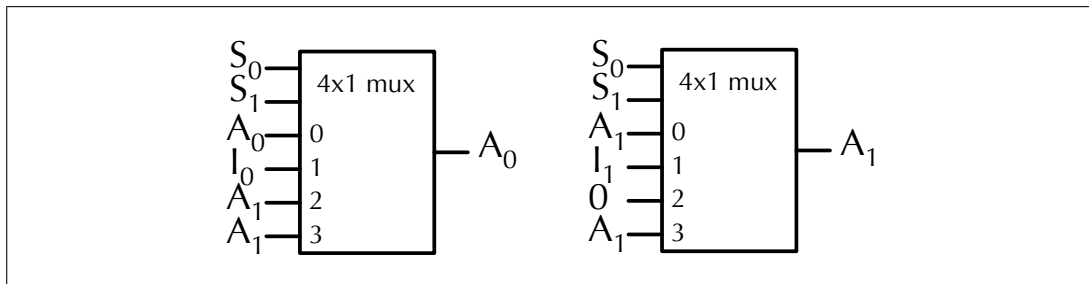
5. (8 marks) Using packages such as decoders, encoders, multiplexers and D flip flops, draw the logic diagram of a 2-bit, divide-by-two register. Use control inputs of 0 to leave the value unchanged, 1 to load a new value, 2 to divide an unsigned number by 2 and 3 to divide a signed, two's complement number by 2. Be sure to carefully label packages and their inputs and outputs. (Hint: remember that there is an easy way to divide an integer by two.)




6. (12 marks) Design a two-bit counter with input C and output E . When $C = 0$, the counter moves to the closest *odd* number *greater than or equal to* its current value (e.g., 2 moves to 3; 3 stays at 3). When $C = 1$, the counter moves to the closest *even* number *greater than* its current value — or to 0 if the current value is 2 or 3 — (e.g., 0 moves to 2; 1 moves to 2); consider 0 to be even. The output E should be 1 when the counter value is even and 0 otherwise. Use D flip flops (recall that the next state of a D flip flop is equal to its input).

6a. Draw the state diagram.

6b. Draw the excitation table.

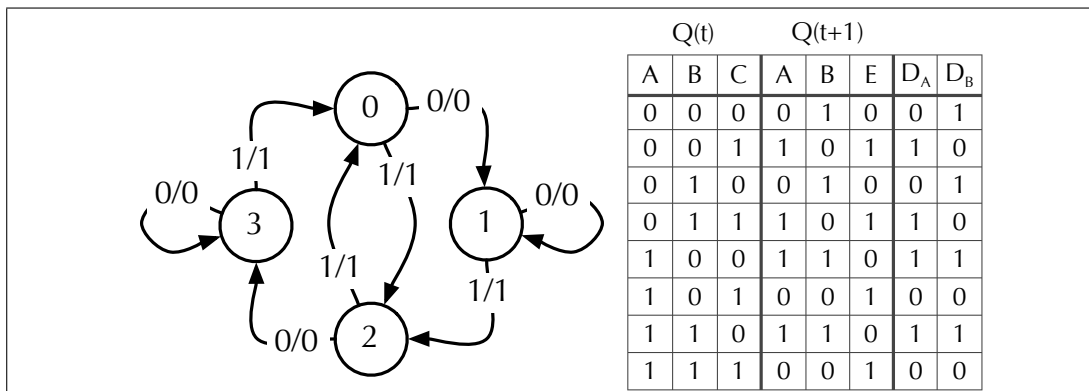

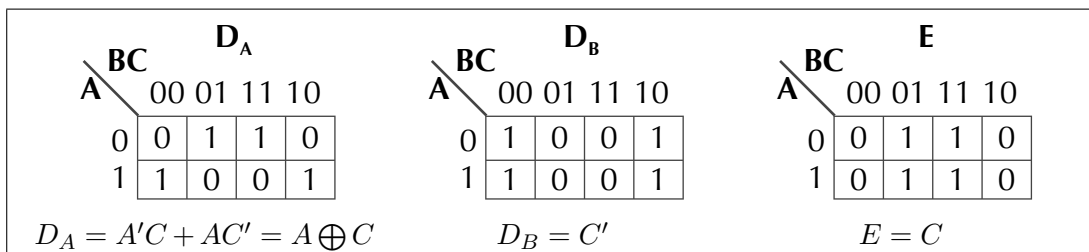6c. Draw all required k-maps and boolean functions.



6d. Draw the circuit.

